

Sequential Logic Circuits Part-II

Assignment

Q.1- Draw neat diagram of R-S flip Flop.

Q2. Write Truth table of R-S flip-Flop.

Q3. Draw neat diagram of R-S flip Flop using Preset and Clear inputs.