

Sequential Logic Circuits Part-I (Latches)

Assignment

Q.1- Write truth table of R-S latch using NAND and NOR gate.

Q2. Explain R-S latch using NAND gate.

Q3. Explain R-S latch using NOR gate.